

Table 4-3: Summary of op-amp circuits.

Op-Amp Circuit	Block Diagram
(a)	Noninverting Amp (v_o independent of R_s)
(b)	Inverting Amp
(c)	Inverting Summing Amp
(d)	Subtracting Amp
(e)	Voltage Follower / Buffer (v_o independent of R_s and R_L)
(f)	Noninverting Summing Amp